

# Problem Set 5

Magson Gao (magson@mit.edu)

6.111 Fall 2018

September 23, 2018

## 1 Problem A

 
 


Figure 1.1: The finite state machine diagram for the given system.

## 2 Problem B

Code:

```

module mem_controller(
    input      clk_in ,
    input      req_in ,
    output     ras_out ,
    output     mux_out ,
    output     cas_out
);

localparam STATE_IDLE = 3'b000;
localparam STATE_ROW  = 3'b001;
localparam STATE_MUX  = 3'b011;
localparam STATE_COL  = 3'b010;
localparam STATE_HOLD = 3'b110;

reg [2:0] state = STATE_IDLE;

assign ras_out = (state == STATE_IDLE);
assign mux_out = ~((state == STATE_IDLE) | (state == STATE_ROW));
assign cas_out = ((state == STATE_IDLE) | (state == STATE_ROW) | (state == STATE_MUX));

// state machine
always @(posedge clk_in)
begin
    case (state)
        STATE_IDLE : state <= req_in ? STATE_ROW : STATE_IDLE;
        STATE_ROW  : state <= STATE_MUX;
        STATE_MUX  : state <= STATE_COL;
        STATE_COL  : state <= STATE_HOLD;
        STATE_HOLD : state <= STATE_IDLE;
    endcase
end
endmodule

```

## Testbench:

```

`define assert(signal, value) \
    if (signal != value) \
    begin \
        $display("ASSERTION FAILED in %m at time %0t: signal != value", $time); \
    end

module mem_controller_tb;
    reg      clk;
    reg      req;
    wire     ras;
    wire     mux;
    wire     cas;
    reg [2:0] clk_counter;

    initial
    begin
        $dumpfile("test.vcd");
        $dumpvars(0, mem_controller_tb);
        clk      = 0;
        clk_counter = 0;
        req      = 0;

        #2;
        req = 1;

        #11;
        req = 0;
        #50;
        $finish;
    end

    mem_controller m1(
        .clk_in      (clk),
        .req_in      (req),
        .ras_out     (ras),
        .mux_out     (mux),
        .cas_out     (cas)
    );

    always @(posedge clk)
    begin
        if ((clk_counter > 0) | ((req == 1) & (clk_counter == 0)))
        begin
            clk_counter = clk_counter + 1;

            if (clk_counter == 1)
            begin
                `assert(ras, 0);
                `assert(mux, 0);
                `assert(cas, 1);
            end
            else if (clk_counter == 2)
            begin
                `assert(ras, 0);
            end
        end
    end
endmodule

```

```

        'assert(mux, 1);
        'assert(cas, 1);
    end
    else if (clk_counter == 3)
    begin
        'assert(ras, 0);
        'assert(mux, 1);
        'assert(cas, 0);
    end
    else
    begin
        'assert(ras, 0);
        'assert(mux, 1);
        'assert(cas, 0);
        clk_counter = 0;
    end
    end
end
end

always #5 clk = ~clk;
endmodule

```

### 3 Problem C

It is glitch free as the states are encoded using grey codes, thus all change of states except from state hold to state idle requires only one bit change. For state hold to state idle there are two possible glitches: 110 to 100 to 000 or 110 to 010 to 000. In both cases the intermediate meta-state has identical output values to the initial hold state. Thus no output glitches occur.

### 4 Problem D

