

# Problem Set 5

Magson Gao (magson@mit.edu)

6.111 Fall 2018

September 27, 2018

## 1 Problem A

 
 


Figure 1.1: The finite state machine diagram for the given system.

## 2 Problem B

Code:

```

module mem_controller(
    input      clk_in ,
    input      req_in ,
    output     ras_out ,
    output     mux_out ,
    output     cas_out
);

localparam STATE_IDLE = 4'b1010;
localparam STATE_ROW  = 4'b0010;
localparam STATE_MUX  = 4'b0110;
localparam STATE_COL  = 4'b0100;
localparam STATE_HOLD = 4'b0101;

reg [3:0] state = STATE_IDLE;

assign ras_out = state[3];
assign mux_out = state[2];
assign cas_out = state[1];

// state machine
always @(posedge clk_in)
begin
    case (state)
        STATE_IDLE : state <= req_in ? STATE_ROW : STATE_IDLE;
        STATE_ROW  : state <= STATE_MUX;
        STATE_MUX   : state <= STATE_COL;
        STATE_COL   : state <= STATE_HOLD;
        STATE_HOLD  : state <= STATE_IDLE;
        default     : state <= STATE_IDLE;
    endcase
end
endmodule

```

## Testbench:

```

`define assert(signal , value) \
    if (signal != value) \
    begin \
        $display("ASSERTION FAILED in %m at time %0t: signal != value", $time); \
    end

module mem_controller_tb;
    reg      clk;
    reg      req;
    wire     ras;
    wire     mux;
    wire     cas;
    reg [2:0] clk_counter;

    initial
    begin
        $dumpfile("test.vcd");
        $dumpvars(0,mem_controller_tb);
        clk      = 0;
        clk_counter = 0;
        req       = 0;

        #2;
        req = 1;

        #11;
        req = 0;

        #50;
        $finish;
    end

    mem_controller m1(
        .clk_in      (clk),
        .req_in      (req),
        .ras_out     (ras),
        .mux_out     (mux),
        .cas_out     (cas)
    );

    always @(posedge clk)
    begin
        if ((clk_counter > 0) | ((req == 1) & (clk_counter == 0)))
            begin
                clk_counter = clk_counter + 1;

                if (clk_counter == 1)
                    begin
                        `assert(ras, 0);
                        `assert(mux, 0);
                        `assert(cas, 1);
                    end
                else if (clk_counter == 2)
                    begin

```

```

        'assert(ras, 0);
        'assert(mux, 1);
        'assert(cas, 1);
    end
    else if (clk_counter == 3)
    begin
        'assert(ras, 0);
        'assert(mux, 1);
        'assert(cas, 0);
    end
    else
    begin
        'assert(ras, 0);
        'assert(mux, 1);
        'assert(cas, 0);
        clk_counter = 0;
    end
    end
end
end

always #5 clk = ~clk;
endmodule

```

### 3 Problem C

Outputs are encoded in the state which is synchronous, thus no glitches occur.

### 4 Problem D

